

## **Module - 4**

### **Feedback**

### **Concept of Feedback**

The process of combining a fraction of output energy back to the Input is called the feedback.


#### **Positive and Negative feedback**

When the feedback is in phase with the Input signal, it is called positive or regenerative feedback. Positive feedback causes excessive distortion and Instability.

The capability of Increasing the power of the original signal it is used in oscillator Circuits. When the feedback is in phase opposition to the Input signal, it is called Negative feedback or degenerative feedback.

Negative feedback reduces amplifier gain but it has numerous advantages (gain stability, reduction in non-linear distortion, Reduction in noise, Increase in bandwidth, Increase in Input Impedance and decrease in output Impedance) and is frequently used in amplifier circuits.

#### **Negative feedback Amplifier**

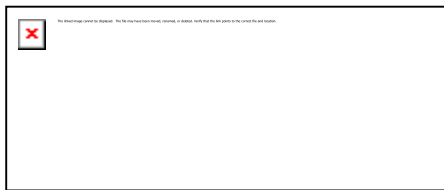

An Amplifier has a voltage gain  $A$  and output voltage  $V_{out}$  is applied to a feedback network which reduce  $V_{out}$  by a factor  $A$  to give a feedback voltage  $V_f$ . The feedback network also ensures that feedback voltage  $V_f$  is in phase opposition to Input Signal voltage  $V_s$ .

$$V_{in} = V_s - V_f$$

A feedback amplifier consists of two parts. An Amplifier and a feedback network is to return a fraction of the output energy to the Input of the Amplifier.

The feedback may be classified as voltage feedback and current feedback. In voltage feedback the energy feedback to the Input terminal is proportional to the Output voltage. while in Current feedback, the energy feedback to the Input terminal is proportional to the Current through load.

Both voltage and Current Can be feedback to the Input either in series or in parallel resulting in four basic feedback connections

1. **Voltage Series feedback**
2. **Voltage Shunt feedback.**
3. **Current Series feedback.**
4. **Current Shunt feedback**

Voltage refers to connecting the output voltage as input to the feedback network and current through the feedback network. Series refers to connecting the feedback signal in series with the input signal voltage and shunt refers to connecting the feedback signal in parallel with an Input Current source.

### **Effect of feedback on Amplifiers**

For an ordinary Amplifier, (without feedback) the voltage gain equals the ratio of output voltage and input voltage.

voltage gain,  $A = \frac{V_{out}}{V_{in}}$

**This gain is called open - loop gain**

Let the fraction of the output voltage  $V_{out}$  be supplied back to the Input and the open loop gain ( $A = \frac{V_{out}}{V_{in}}$ ).

$$V_{in}$$

Now the Input voltage becomes

$$V_{in} = V_s + V_f = V_s + B V_o \text{ (Positive feedback)}$$

$$V_{in} = V_s - V_f = V_s - B V_o \text{ (Negative feedback)}$$

i.e  $V_{in} = V_s \pm B V_o$  (depending on whether the feedback voltage is in phase or out of phase to the Input signal voltage).

Voltage gain,  $A = \frac{V_{out}}{V_{in}}$

$$V_{in}$$

$$V_{out} = A V_{in}$$

Sub  $V_{in} = V_s - B V_o$  (negative feedback)

$$V_{out} = A (V_s - B V_o)$$

$$V_o = A V_s - A B V_o$$

$$V_o + A B V_o = A V_s$$

$$V_o (1 + A B) = A V_s$$

$$\frac{V_o}{V_s} = \frac{A}{1 + A B}$$

Voltage gain with Negative feedback,  $A_f = \frac{V_{out}}{V_s}$

$$V_s$$

$$A_f = \frac{A}{1 + A B}$$

Similar voltage gain with positive feedback,  $A_f = \frac{A}{1 - A B}$

The term AB is called feedback factor where as B is known as feedback ratio.

### **Advantages of Negative feedback**

There are numerous advantages of negative feed back

1. **Gain Stability**
2. **Reduced Non - linear Distortion.**
3. **Reduced Noise.**
4. **Increased Bandwidth**
5. **Increased Input Impedance.**
6. **Reduced Output Impedance.**

### **Explanation**

#### **1) Stabilization of Gain with Negative feedback**

The variation of temperature supply voltage ageing of Components or variation in Transistor parameters with replacement are some of the factors that affects the gain of an amplifier and cause it to change. The over all gain Independent of these variations if negative feedback is used.

The voltage gain with negative feedback

$$A_f = \frac{A}{1 + AB}$$

#### **2) Feedback**

Noise in an amplifier is reduced in the same way as distortion. distortion is usually Introduced in the last stage of the amplifier. The noise can be reduced by negative feedback only if its source the with in the feedback loop after the first stage.

#### **3) Effect of Negative feedback on Gain and Bandwith**

In practical amplifiers the open - loop gain drops off at higher frequencies due to the device and Circuit Capacitance.

The Amplifier with negative feedback has a larger bandwidth. Negative feedback in amplifier has indeed the effect of maintaining the gain gets reduced, the band width is Increased.

#### 4) Effect of feedback on Impedance

##### 1. Input Impedance

##### Effect of voltage series feedback

$$\underline{V_s} = Z_i (1+AB)$$

$$I_i$$

$$\therefore Z_{if} = Z_i (1 + AB)$$

##### Effect of voltage shunt feedback

$$Z_{if} = \frac{\underline{V_i}}{I_s} = \frac{\underline{V_i}}{I_i + I_f}$$

$$\therefore Z_{if} = \frac{Z_i}{1 + AB}$$

##### Out put Impedance

##### Effect of voltage Series feedback

$$Z_{of} = \frac{\underline{V}}{I}$$

$$Z_{of} = \frac{Z_o}{1 + AB}$$

#### 5) Stability in feedback Amplifiers

In Negative feedback, the feedback Signal is subtracted from the applied signal. The Amplifier must process a signal which is the sum of the Input and feedback signal causing the output to be become quite large


$$A_f = \frac{A}{1 + AB}$$

This unbounded Output results in a Condition called Instability, which must be avoided in feedback Amplifiers.
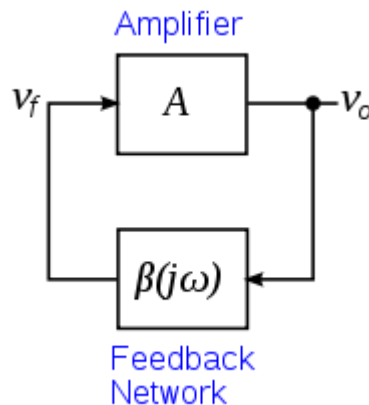
## Oscillators

An oscillator is a type of feedback Amplifier in which part of the output is feedback to the Input via a feedback Circuit. In the signal feedback is of proper magnitude and phase, the circuit produces a periodic waveform on its output with Oscillator block Diagram only dc power supply voltage as an Input

The feedback is positive most Oscillator use positive feedback. The closed loop gain of the Amplifier is denoted by  $A_v$ .



$$V_d = V_f + V_{in}$$

$$V_o = A_v V_d$$

$$V_f = B V_o$$

For positive feedback

$$\frac{V_o}{V_{in}} = \frac{A_v}{1 - A_v B}$$

$$V_{in} = 0 \text{ \& } V_o \neq 0$$

$$A_v B = 1$$

**This is the condition for Oscillation.**

### **The Two requirement for oscillation**


(1) The Magnitude of the loop gain  $A_v B$  must be at least 1

(2) The total phase shift of the loop gain  $A_v B$  must be equal to 0 or 360 degree. This condition is known as **Barkhausen Condition for Oscillation.**

### **Frequency Stability**

The ability of the Oscillator Circuit to Oscillate at one exact frequency is called **frequency stability**. A number of factors may cause change in oscillator frequency. They are Temperature change, change in the dc power supply.

### **RC - phase shift Oscillator**

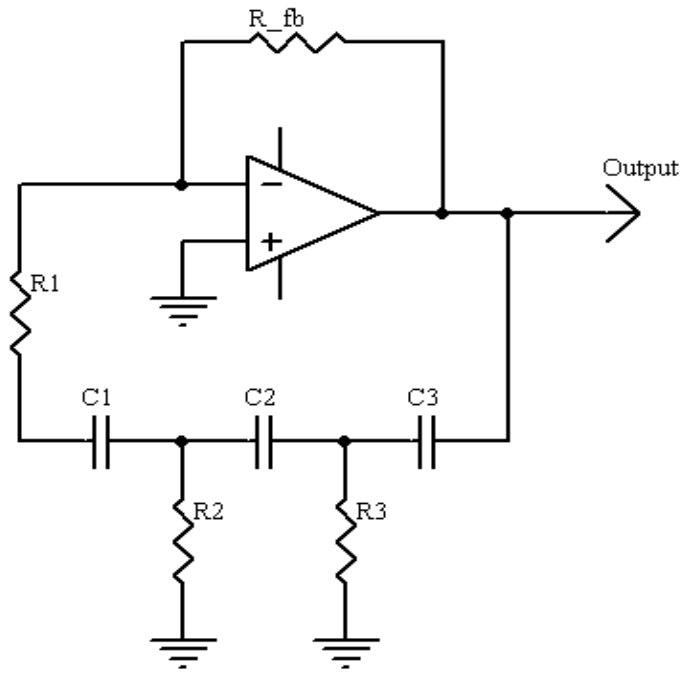

### **Working**

The circuit consist of an op- Amp and three RC network.


The Op-amp Provides a phase shift because op-Amp the inverting mode configuration of  $180^\circ$  and An Additional  $180^\circ$  phase shift is provided by the Three RC. The feedback gain

$$B = \frac{1}{29}$$

So the circuit will Oscillate if  $A > 29$



## Wein bridge Oscillator

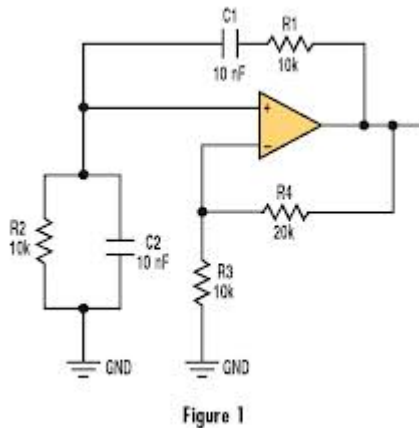

## Working


Wein bridge Oscillator can be viewed as a non inverting amplifier configuration with the Input signal fed back from the Output through the feedback Circuit. The Circuit to produce a sinusoidal output the phase shift around the feedback loop must be equal to unity. The frequency of Oscillation.

## Oscillator with LC feedback Circuits

The RC feedback Oscillator, wein bridge Oscillator are suitable for frequency of about 1MHz, LC feedback elements are used in oscillator that require higher frequency of oscillation. Several types of LC feedback Oscillator are used

- 1) **Colpitts**
- 2) **Hartley**
- 3) **Crystal oscillator.**

### 1) Colpitts Oscillator

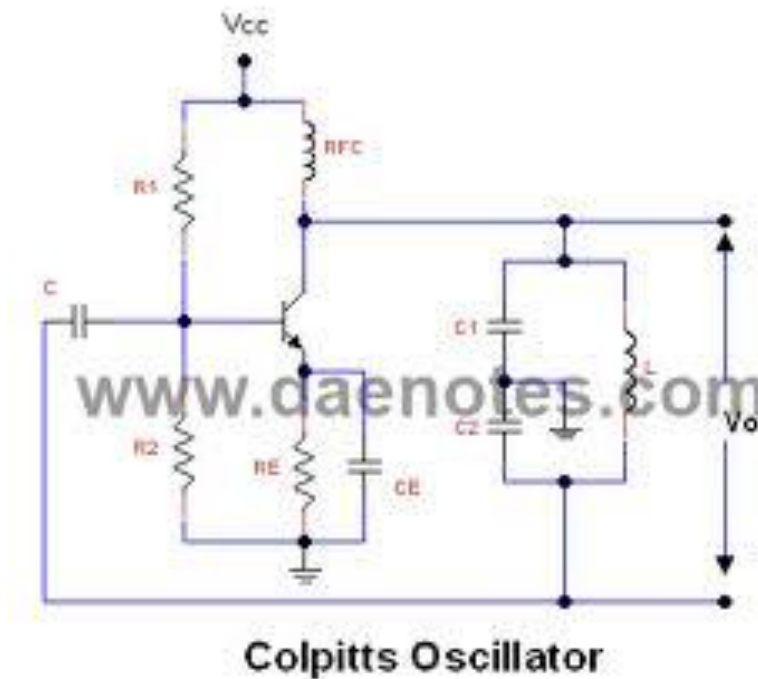

The Oscillator uses an LC Circuit in the feedback loop to provide the necessary phase shift and to act as a Resonant filter that phases only the desired frequency of Oscillation.

The frequency of Oscillation in the resonant frequency of LC Circuit and is established by the values of  $C_1$ ,  $C_2$  and  $L$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

**Condition for oscillation and startup**

The Attenuation  $B$  of the Resonant feedback Circuit in the Colpitt's oscillator is determined by the values of  $C_1$  and  $C_2$ .


The voltage across  $C_2$  is the oscillator output voltage ( $V_{out}$ ) and the voltage developed across  $C_1$  is the feedback voltage ( $V_f$ )

$$\begin{aligned} \text{Attenuation } B &= \frac{V_f}{V_{out}} = \frac{IX_{C1}}{IX_{C2}} \\ &= \frac{X_{C1}}{X_{C2}} \\ B &= \frac{C_2}{C_1} \end{aligned}$$

The condition for oscillation  $A_v B = 1$

## Hartley Oscillator

### Circuit Diagram

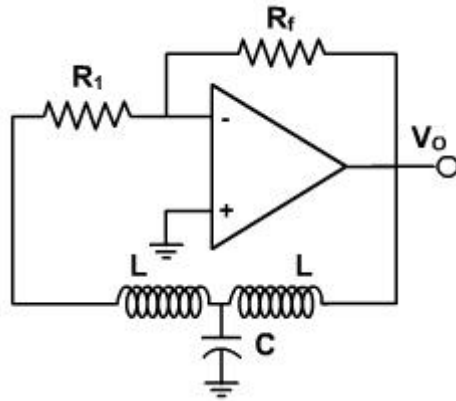

### Working

The Hartley Oscillator consists of two series inductors and a parallel capacitor.

In this circuit, the frequency of oscillation

The attenuation,  $B$  of the feedback circuit

$$B = \frac{L_1}{L_2}$$

To assure start-up of oscillation  $A_v$  must be greater than  $\frac{1}{B}$

## Crystal Controlled Oscillator

The most stable and accurate type of feedback oscillator uses a piezoelectric crystal in the feedback loop to control the frequency.


### The piezoelectric Effect

When a changing mechanical stress is applied across the crystal to cause it to vibrate, a voltage develops at the frequency of mechanical vibration

eg: Quartz Crystal

When an ac voltage is applied across the crystal it vibrates at the

frequency of applied voltage.

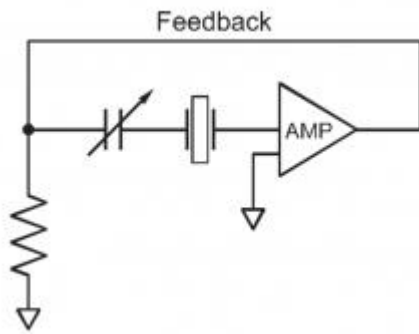

A Great advantage of the crystal is that it exhibits a very high Q.

The Impedance of the crystal is minimum at the series resonant frequency, thus providing maximum feedback. The Fundamental frequency depends on the crystal's mechanical dimensions, type of cut, and inversely proportional to the thickness of the crystal slab

For most crystals, the upper limit is less than 20MHz. for higher frequencies the crystal must be operated in the Overtone mode.